1

FPGA LAB Assignment 1

Yenigalla Samyuktha EE20MTECH14019

Download all codes from

https://github.com/EE20MTECH14019/FPGA -14019/tree/main/Assignment _1

and latex-tikz codes from

https://github.com/EE20MTECH14019/FPGA -14019/tree/main/Assignment_1

1 Problem

(CBSE/CS/2015-1/6.c) Derive a Canonical POS expression for a Boolean function F, represented by the following truth table 0:

P	Q	R	F(P,Q,R)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

TABLE 0: Truth table for Function F

2 Solution

From the truth table 0, the function F(P, Q, R) can be represented in the Canonical POS form as follows:

As F is logic 0 for four input combinations, the corresponding max terms are,

$$M_1 = (P + Q + \bar{R}) \tag{2.0.1}$$

$$M_2 = (P + \bar{Q} + R) \tag{2.0.2}$$

$$M_5 = (\bar{P} + Q + \bar{R}) \tag{2.0.3}$$

$$M_6 = (\bar{P} + \bar{Q} + R) \tag{2.0.4}$$

And the Canonical POS expression can be expressed using these max terms as.

$$F = M_1 \cdot M_2 \cdot M_5 \cdot M_6 \tag{2.0.5}$$


$$F = \prod M(1, 2, 5, 6) \tag{2.0.6}$$

$$F = (P + Q + \bar{R}) \cdot (P + \bar{Q} + R) \cdot (\bar{P} + O + \bar{R}) \cdot (\bar{P} + \bar{O} + R)$$

$$(2.0.7)$$

Implementation using two input NAND gates

 Minimizing the function (2.0.7) using K-maps,



From the K-Map, the minimized POS form is,

$$F = (Q + \bar{R}) \cdot (\bar{Q} + R) \tag{2.0.8}$$

$$F = \bar{Q} \cdot \bar{R} + Q \cdot R \tag{2.0.9}$$

Using Demorgan's law,

$$F = \overline{(\bar{Q} \cdot \bar{R}) \cdot (\bar{Q} \cdot \bar{R})}$$
 (2.0.10)

Now, implementing the Boolean function F in (2.0.10) using two input NAND gates:

 


Fig. 0: Implementation using two input NAND gates